 



Lab2 ALU

106000215 江承翰

需要用NAND gate實作部分的電路圖




AND gate

 


OR gate

需要用NAND gate實作部分的電路圖

 


NOT gate

 


XOR gate

Remark: A' and B' are also made by NAND gate using the way above

需要用NAND gate實作部分的電路圖

 

XNOR gate

 

NOR gate

ncverilog 執行結果(最終make syn)

```
tsmc13.XOR3X1:v <0x0ec0956a>
  streams: 10, words: 1277
worklib.ALU:v <0x4c2c6a61>
  streams: 0, words: 0
worklib.AND:v <0x0f5bfce5>
  streams: 0, words: 0
worklib.Arbitrator:v <0x3d526739>
  streams: 0, words: 0
worklib.Decoder:v <0x48f2d2ce>
  streams: 0, words: 0
worklib.NOR:v <0x669949ab>
  streams: 0, words: 0
worklib.tb:v <0x234f6d74>
  streams: 8, words: 81468
Building instance specific data structures.
Loading native compiled code: ..... Done
Design hierarchy summary:
      Instances  Unique
Modules:         1078    56
Primitives:      2592     8
Timing outputs:  1244    17
Registers:        7      7
Scalar wires:    1252     -
Expanded wires:   68      3
Always blocks:    1      1
Initial blocks:   3      3
Cont. assignments: 0      5
Pseudo assignments: 4      4
Interconnect:    2967     -
Simulation timescale: 1ps
Writing initial simulation snapshot: worklib.tb:v
Loading snapshot worklib.tb:v ..... Done
*Verdi3* Loading libsscore_ius141.so
*Verdi3* : Enable Parallel Dumping.
ncsim> source /usr/cad/cadence/INCISIV/cur/tools/inca/files/ncsimrc
ncsim> run
```

```
score =          41 / 41
Congratulations!!!!
You pass all of the testcases. :)))
```

```
Simulation complete via $finish(1) at time 1410 NS + 0
./ALU_tb.v:479 $finish;
ncsim> exit
TOOL: ncverilog 14.10-s005: Exiting on Apr 18, 2019 at 15:16:37 CST (total: 00:00:02)
(END)
```

Report Area

```
1
2 *****
3 Report : area
4 Design : ALU
5 Version: K-2015.06-SP1
6 Date   : Thu Apr 18 15:14:22 2019
7 *****
8
9 Library(s) Used:
10
11     slow (File: /theda21_2/CBDK_IC_Contest/cur/SynopsysDC/db/slow.db)
12
13 Number of ports:          400
14 Number of nets:          1606
15 Number of cells:         1077
16 Number of combinational cells: 1065
17 Number of sequential cells:    1
18 Number of macros/black boxes:  0
19 Number of buf/inv:          202
20 Number of references:        39
21
22 Combinational area:      13185.403310
23 Buf/Inv area:            879.253186
24 Noncombinational area:   0.000000
25 Macro/Black Box area:   0.000000
26 Net Interconnect area:   undefined (No wire load specified)
27
28 Total cell area:         13185.403310
29 Total area:              undefined
30
```


問題討論

關於Arbiter

- ▶ 在查過維基百科後，大概了解Arbiter(仲裁器)大致上是在多CPU時常用的Unit，負責在有多個程序同時索求電腦資源或記憶體時，將資源優先分配給優先度較高的程序。這次實作的find first bit arbiter就是類似的概念，以A的bit順序模擬處理器程序的優先順序。

關於always block

- ▶ 助教在講解時有跟我們說，always block中盡量不要針對多個變數做控制，但我在實作時並沒有考慮到這點，導致使用舊版的testbench會在A-B時出現unexpected result(左邊的幾個bit會變成1)。雖然使用新版的testbench之後問題已經改善，這次也來不及改，但我以後會養成良好的coding習慣，將不同的變數分開處理。

關於makefile

- ▶ 這次我有在助教的makefile中加入了一些自訂的指令，讓make cleaning變得更好用些(加入*.sdf, Report_area.txt, ALU_syn.v，讓cleaning清得更乾淨)，另外想順便請問一下助教：
 - ▶ 在SRC_syn中的第三行(-v /theda21_2/CBDK_IC_Contest/...)的意義
 - ▶ header.v的意義
- ▶ 由於以上功能這次並沒有用到，所以把疑問放在這裡

Thank you